

$$\underline{f_0 = \sqrt{f_1 f_2}} \quad \underline{\text{proof:}}$$

at half power frequencies, the circuit current becomes

$$\frac{1}{\sqrt{2}} I_0$$

circuit impedance at resonance = R .

\therefore circuit impedance at half power frequencies is

$$\sqrt{2} R \quad \left(\because Z = \frac{V}{I} \right)$$

$$\Rightarrow \sqrt{2} R = \sqrt{R^2 + X^2} \Rightarrow R = X \text{ at } f_1 \& f_2$$

at f_1 :

$$X_1 = \omega_1 L - \frac{1}{\omega_1 C} = -R \quad \therefore X_L < X_C \text{ at } f_1$$

$$\omega_1 L + R - \frac{1}{\omega_1 C} = 0 \Rightarrow \omega_1^2 + \frac{R}{L} \omega_1 - \frac{1}{LC} = 0$$

$$\Rightarrow \omega_1 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 + \omega_0^2} \quad \text{①}$$

$$\text{where } \alpha = \frac{R}{2L} \quad \& \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

as -ve freq is not possible

$$\text{①} \Rightarrow -\alpha + \sqrt{\alpha^2 + \omega_0^2} \quad \text{②}$$

at f_2 :

$$X_2 = \omega_2 L - \frac{1}{\omega_2 C} = +R \Rightarrow \omega_2 L - R - \frac{1}{\omega_2 C} = 0$$

$$\Rightarrow \omega_2^2 - \frac{R}{L} \omega_2 - \frac{1}{LC} = 0 \Rightarrow \omega_2 = \alpha + \sqrt{\alpha^2 + \omega_0^2} \quad \text{③}$$

$$\text{②} \times \text{③} \Rightarrow \omega_1 \omega_2 = \alpha^2 + \omega_0^2 - \alpha^2 \Rightarrow \omega_1 \omega_2 = \omega_0^2$$

$$\Rightarrow (2\pi f_1) (2\pi f_2) = (2\pi f_0)^2 \Rightarrow$$

$$\boxed{f_0 = \sqrt{f_1 f_2}}$$

