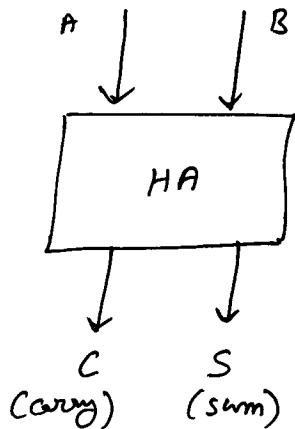


Half adder


→ The circuit which adds two bits, ignoring the carry from the previous bit addition is called half adder.

→ It has two inputs and two outputs.

→ 2 inputs are 2 bits to be added and 2 outputs are sum & carry



A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

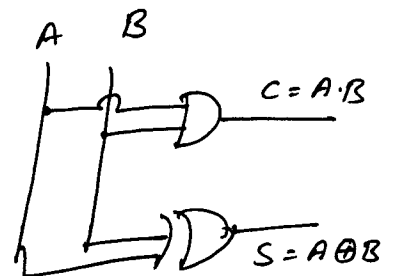

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = A \cdot B$$

Full adder:-


→ Full adder is meant to add two bits along with carry from the former bit addition.

ex:

$$\begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 \begin{array}{c} S \\ C_i \end{array} \begin{array}{c} 0101 \\ \nearrow \nearrow \nearrow \nearrow \\ 1010 \end{array} \\
 \hline
 \underline{\underline{Sum}} \quad \underline{\underline{11001}}
 \end{array}$$

except LSB, full adder is repeated for remaining bits

②

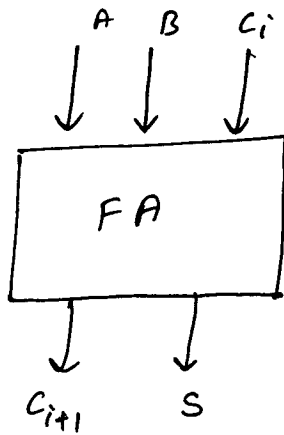

A	B	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$S = A \oplus B \oplus C_i$ \therefore sum = 1 when input has ~~even~~ odd number of 1's.

$$C_{i+1} = \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i$$

$$(+ \overline{ABC_i} + \overline{A\bar{B}C_i})$$

$$= BC_i + AC_i + AB$$

$$C_{i+1} = AB + BC_i + AC_i = \underline{(A \oplus B)C_i + AB}$$

